## RECENT IC ANNOUNCEMENTS **VENDOR PART NUMBER DESCRIPTION** PRICE/QUANTITY **AVAILABILITY DSP** BDSP9124 Butterfly Transform-based digital signal processor is available at 60 MHz, performs \$390/10,000 Prod.—Now 360.892.5597 1,024-point complex FFTs in 53 microseconds, with 8-24-bit precision. TMS320C82 New DSP features two DSP cores, microcontroller, FPU, and caches, with \$82/25,000 Samples-Now 800.477.8924 50-MHz clock rate; DRAM interface handles EDO, VRAM, and SDRAMs. Prod.—1Q97 MICROPROCESSOR HCS360 Microchip Tiny microcontrollers act as Keeloq code-hopping encoders or decoders; \$0.94/25,000 Prod.—Now HCS509 602.786.7668 exceed rolling-code RKE requirements of automobile OEMs; in SOIC-8. **INTERFACE** KB8527A Cordless-telephone circuit contains RF amplifier, receiver, compander, \$1.80/100,000 Prod.—Now Samsung 408.954.7228 and universal PLL to reduce surrounding frequency interference. PI5L100 Quad two-channel LanSwitch circuit replaces mechanical switches or \$1.50/5,000 Prod.—Now Pericom 408.435.0800 relays in networking-switching applications; less than -45 dB crosstalk. NEC Physical-layer chip for ATM handles six 25-Mbps ports, suitable for con-\$66/10,000 Prod.—Now uPD98408 800.366.9782 centrators and switches; supports UTOPIA Level 2; in PQFP-208. ML6680 Micro Linear Fiber-optic transceiver for token-ring networks converts output from \$22.80/1,000 Prod.—Now 408.433.5200 twisted-pair output to fiber-optic waveform at 16 Mbps; in PLCC-28. Gigabit-Ethernet transceiver handles clock and data recovery at 1.25 Gbps VSC7135 Vitesse \$20/10,000 Samples—Now 805.388.3700 with 700-mW (typical) power dissipation; in 14-mm QFP package. Prod.—1Q97 **MEMORY** Parallel E<sup>2</sup>PROM has 16-Kbit capacity, organized as 2K×8, with software M28C17 SGS-Thomson \$2.50/1.000 Prod.—Now write-protect feature, 90-ns access time, and 40-year data-retention time. 617.259.0300 DS1330 Dallas Semi Nonvolatile module with 32K×8 ('30) or 512K×8 ('50) of SRAM, battery \$16.12/1,000 Prod.—Now 214.450.0448 monitor, and CPU-reset circuit; package is compatible with PLCC-68. DS1350 MD904 MoSys Multibank MDRAMs have 4-Mbit ('904) and 10-Mbit ('910) capacity, \$10/1,000 Samples—Now MD910 408.321.0770 for conveniently sized frame-buffer storage for PCs or add-in boards. Prod.-4Q96 MISCELLANEOUS CS7870 Crystal Two 12-bit analog-to-digital converters use SAR methods, offer 100-kHz \$14.95/1,000 Prod.—Now 512.912.3736 CS7875 throughput, 73-dB signal/noise ratio, and consume 75 mW (typical). Audio power amplifier delivers 4×22-W RMS output power (4×33 W by TDA7385 SGS-Thomson \$5.50/10,000 Prod.—Now 617.259.0300 EAIJ standards) in a single package; requires no external capacitors. Quad micropower comparators with on-board reference feature 5-µA LTC144x Linear Technology \$2.70/1,000 Prod.—Now 408.432.1900 quiescent current, 8.5-µA maximum; outputs source 200 µA, sink 20 µA. PROGRAMMABLE LOGIC A32200 Actel FPGA has 20,000-gate capacity and uses both antifuses and SRAM cells for \$225/5,000 Prod.—Now 408.739.1010 configuration; with 2,560 SRAM bits with 5-ns access time; in PQFP-208. SYSTEM LOGIC Sigma Designs EM8000 Single chip integrates MPEG-1 audio and video decoding, X-Y scaling, and \$41/1,000 Prod.—Now 510.770.0100 plug-and-play ISA bus interface for PCs and add-in boards.